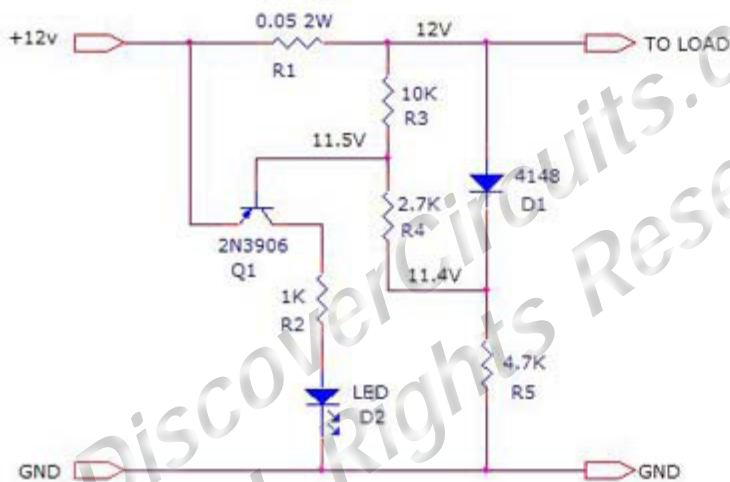


SELECT FOR DESIRED CURRENT TO LIGHT LED

$R1 = 0.1/A$
WHERE A = AMPS



DC CURRENT INDICATOR

4 AMP DETECTION WITH VALUES SHOWN

DESIGNED BY DAVE JOHNSON
DISCOVERCIRCUITS.COM
ALL RIGHTS RESERVED

DRAWN BY: DAVE JOHNSON