



WITH THE ZENERS IN THE CHARGE PUMP CIRCUIT, THIS VOLTAGE CAN BE BOOSTED TO MAYBE 12V.

FLEXIBLE SIGNAL DRIVER CIRCUIT

DRAWN BY: DAVE JOHNSON

DAVID JOHNSON AND ASSOCIATES			
Title FLEXIBLE DRIVER			
Size B	Document Number FLEXDRI3.DSN	Rev A	
Date: Saturday, July 08, 2000		Sheet 1 of 1	